

# Multiple Formulas

Potential difference Voltage	Power	Energy 1	Energy 2
$V = R \times I$	$P = V \times I$	$E = P \times t$	$E = I \times V \times t$

1. What is the power of an appliance if it works on 2.5 A and has a 5 Ω resistor?

$$P = V \times I \quad P = 12.5 \text{ V} \times 2.5 \text{ A} \quad V = R \times I$$

$$P = 31.25 \text{ W} \quad V = 5 \Omega \times 2.5 \text{ A}$$

2. What is the resistance of a resistor if it uses 220 V and 300 W power?

$$R = \frac{V}{I} \quad \frac{220 \text{ V}}{1.36 \text{ A}} = 161.76 \Omega \quad P = V \times I \quad I = \frac{P}{V} \quad \frac{300 \text{ W}}{220 \text{ V}}$$

$$I = 1.36 \text{ A}$$

3. What is the resistance of a resistor if a circuit is on for 20 minutes, used 20 000 J of energy and had 4 A?

$$R = \frac{V}{I} = \frac{4.2 \text{ V}}{4 \text{ A}} = 1.04 \Omega \quad E = I \times V \times t \times 60$$

$$V = \frac{E}{I \times t} = \frac{20000}{4 \times 1200} = 4.2 \text{ V}$$

4. What is the resistance of a resistor if a circuit is on for 2 hours, used 50 000 J of energy and 220 V?

$$R = \frac{V}{I} = \frac{220 \text{ V}}{0.32 \text{ A}} = 687.5 \Omega \quad E = I \times V \times t \quad I = \frac{E}{V \times t} = \frac{50000}{220 \times 7200}$$

5. What is the power of an appliance if it works on 5 A and has a 3.5 Ω resistor?

$$P = V \times I \quad V = R \times I$$

$$17.5 \text{ V} \times 5 \text{ A} = 87.5 \text{ W} \quad V = 3.5 \Omega \times 5$$

$$V = 17.5 \text{ V}$$

6. The resistance of a heating element is 10 Ω and the potential difference (voltage) across its terminals is 120 V. This element is used for 3 hours. How much electrical energy was used during this period?

- A) 4 320 J    B) 259 200 J    C) 1440 000 J    D) 15 552 000 J

$$I = \frac{V}{R} = \frac{120}{10} = 12 \text{ A} \quad E = I \times V \times t$$

$$(12)(120)(10800) \quad \times 3600$$